

# Smart Walking Stick for the Visually Impaired

## Components Required:

Ultrasonic sensor


Arduino

Jumper Wires

Bluetooth terminal

Buzzer

## Circuit Diagram:

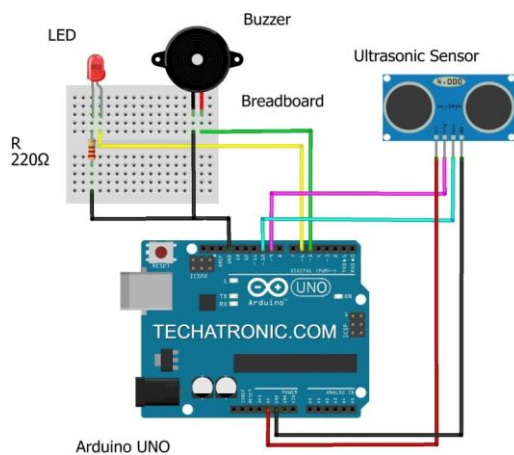

## Procedure:

- Please make the connections according to the given **Smart blind stick circuit diagram**.
- Attach the 5-volts and GND pins of the Arduino to the VCC and GND pins of the ultrasonic sensor.
- Connect the TRIG and ECHO pins of the ultrasonic sensor with the digital-9 and digital-10 pins of the Arduino.
- Join the positive and negative wire of the buzzer with the digital-5 and GND pins of the Arduino.
- Attach the positive leg of the LED with the digital-6 pin of the Arduino and the negative leg of the LED with the GND pin of the Arduino through a 220-ohm resistor.
- You can use a breadboard for making common connections. Power the Arduino board using DC batteries.

## Arduino Code:

```
const int trigPin = 9;  
const int echoPin = 10;  
long duration;
```

```

int distanceCm,
distanceInch;
void setup()
{
  Serial.begin(9600);
  pinMode(trigPin, OUTPUT);
  pinMode(echoPin, INPUT);
  pinMode(6, OUTPUT); // Connect LED Pin D6
  pinMode(5, OUTPUT); // Connect Buzzer Pin D5
}
void loop()
{
  digitalWrite(trigPin, LOW);
  delayMicroseconds(2);
  digitalWrite(trigPin, HIGH);
  delayMicroseconds(10);
  digitalWrite(trigPin, LOW);
  duration = pulseIn(echoPin, HIGH);
  distanceCm= duration*0.034/2;
  distanceInch = duration*0.0133/2;
  Serial.println("Distance: ");
  Serial.println(distanceCm);
  delay (100);
  if(distanceCm < 25) // You can Change the value
  {
    digitalWrite(5, HIGH); // Buzzer ON
    digitalWrite(6, HIGH); // LED ON
  }
  else {
    digitalWrite(5,LOW); // Buzzer OFF
    digitalWrite(6,LOW); // LED OFF
  }
}

```

}  
}

**Output:**

